

ISTANBUL TECHNICAL UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT

BLG 222E
Computer Organization
Project Report

Project NO : 1
Due Date : 12.04.2023
GROUP NO : G37

GROUP MEMBERS:

150200075 : Matay AYDIN
150200096 : Mustafa KIRCI
150200916 : Denis Iurie DAVIDOGLU

SPRING 2023

Contents

1	Introduction	1
2	Project	1
2.1	Part 1	1
2.2	Part 2	3
2.2.1	Part 2a	3
2.2.2	Part 2b	5
2.2.3	Part 2c	8
2.3	Part 3	10
2.4	Part 4	13
3	Conclusion	16

1 Introduction

Computers can be different by their architecture, instruction sets, peripherals and performance. However, the processors lying on their core perform same basic functions: fetching data and instructions from memory, carry logic operations, adding, multiplying, comparing, outputting results to the system bus, and so on. All of these are done using multiplexers, registers and arithmetic logic units. In this project, the aim is to design the most basic ALU system in Verilog HDL. All the required modules are described at the behavioral level, and checked detaily in testbenches. In part one, n-bit register with four functions is presented, which will be used in all succeeding parts. In general, the entire system is just a large network of registers; therefore, it is crucial. In the second part, three different register files are derived from the main register module, which will be used to store instructions, temporary data, as well as registers for executing a program in the correct order. Part three is the brain of the system, the arithmetic logic unit, which performs operations on two values, gives the result of computation, as well as flags for interpreting the data. In the last fourth part, all modules are combined to create a fully-functional computer, that connects to an external memory.

Responsibility distribution between team members is as follows:

- **Part 1:** Denis
- **Part 2a:** Denis
- **Part 2b:** Mustafa
- **Part 2c:** Denis
- **Part 3:** Matay
- **Part 4:** Mustafa
- **Report:** Denis, Mustafa, Matay


2 Project

2.1 Part 1

To get started with modeling on the register-transfer level, the most basic unit, the register, is needed. Plain register that Verilog offers is not enough, since we want a structure that will be synchronous with system clock, have enable input, two-bit function select input, load input data lines and output data lines. The table below describes the behaviour of our register:

E	FunSel	Q^+
0	ϕ	Q (retain value)
1	00	0 (Clear)
1	01	I (Load)
1	10	$Q - 1$ (Decrement)
1	11	$Q + 1$ (Increment)

 Moreover, for this register to be universal, it should have a parametrized number of data lines. The block diagram on the left is equivalent to the Verilog code on the right.



(a) n-bit register diagram

```

≡ part1.v
1  module register #(
2  parameter NBits = 16
3  ) (
4  input          clk,
5  input[1:0]     funsel,
6  input          e,
7  input[NBits-1:0] i,
8  output[NBits-1:0] q
9  );

```

(b) Module definition in Verilog

Although not drawn in the diagram, the clock signal is also an input, whose rising edge triggers operations, described in the function table given above. These simple rules were translated to Verilog too, by using statements such as **always**, **if** and **case**. Module's testbench creates a 4-bit register instance, which is a reasonable size for testing. Register is simulated for all functions, i.e. clear, load, decrement and increment:

 


Figure 2: Load and clear test (part 1)

 


Figure 3: Decrement test (part 1)

 


Figure 4: Increment test (part 1)

Note: In the testbench, enable signal was always high and was not tested for low value, since the implementation already guarantees changes in output only for the high value.


2.2 Part 2

2.2.1 Part 2a

In this part, a 16-bit instruction register design is provided. While the internal structure contains a 16-bit instance of the register from previous part, data is coming in in halves, 8 bit at a time. The selection between bits is done by an additional $\bar{\mathbf{L}}/\mathbf{H}$ input, and the other functionalities remain the same, as described in the table:

$\bar{\mathbf{L}}/\mathbf{H}$	\mathbf{E}	\mathbf{FunSel}	\mathbf{IR}^+
ϕ	0	$\phi\phi$	IR (Retatin Value)
ϕ	1	00	0 (Clear)
0	1	01	$\mathbf{IR}(7-0) \leftarrow \mathbf{I}$ (Load LSB)
1	1	01	$\mathbf{IR}(15-8) \leftarrow \mathbf{I}$ (Load MSB)
ϕ	1	10	$\mathbf{IR}-1$ (Decrement)
ϕ	1	11	$\mathbf{IR}+1$ (Increment)

 From the graphical representation on left, Verilog module is derived:



(a) 16-bit instruction register diagram

```

part2a.v
3  module IR_16_bit (
4      input      clk,
5      input[7:0] i_half,
6      input[1:0] funsel,
7      input      e,
8      input      l_h,
9      output[15:0] ir_out
10 );

```

(b) Module definition in Verilog

Clock signal is not connected to the internal n-bit register module directly. Instead, it uses a delayed clock, so that there are no race conditions with the parent module. We want first to process the inputs in the parent module, then after a delay, process them in the internal one. As a result, the output of instruction register changes slightly after the main clock's rising edge:



Figure 6: Delayed clock (part 2a)

Testbench includes similar tests as for n-bit register module:

 


Figure 7: Load and clear test (part 2a)

 


Figure 8: Decrement test (part 2a)

 


Figure 9: Increment test (part 2a)

2.2.2 Part 2b

The purpose of the register file (RF) module is to control the 4 8-bit general purpose registers and 4 8-bit temporary registers. To achieve this, module has 6 inputs. Those are: i, O1Sel, O2Sel, FunSel, RSel and TSel. These i input wire provides the bits that will be loaded into the active registers if the given FunSel allows it. O1Sel and O2Sel selects the outputs of registers for the output of the module. FunSel determines which operation the active registers will compute. Lastly, RSel and TSel are used to determine active registers. OSel inputs work as if they represent the index of the register. Register selection inputs works as if each bit represents the enable-disable state of the corresponding register. The details are given in the project description file.

Registers inside this module are connected to delayed clock. The reason for this implementation detail is to avoid the race conditions. If same clock is given to registers, undetermined behaviours occurs at each positive clock edge.

The schematics of register file is as below.

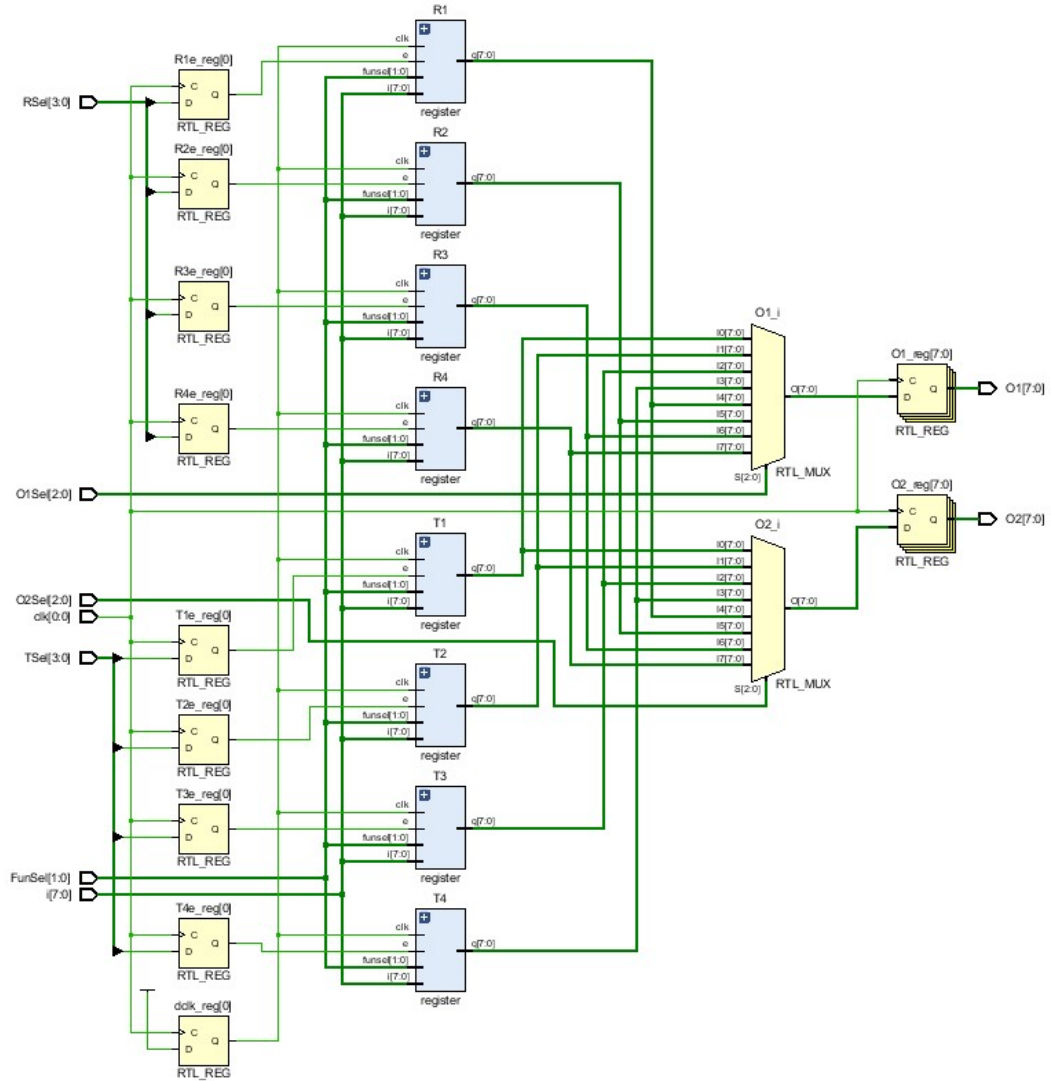


Figure 10: Schematics of Register File

For testing the RF module, FunSel is given as 01 so that module is initialized correctly. To initialize every register inside the RF, ALL registers are enabled. RSel = 1111, TSel = 1111, FunSel = 01

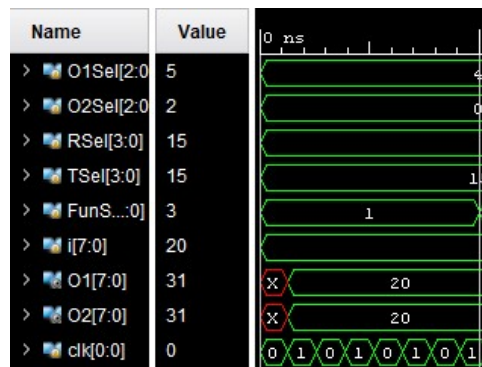


Figure 11: Loading Test (part 2b)

Testing incrementing while all registers are enabled.

 


Figure 12: Increment Test (part 2b)

Testing decrementing while all registers are enabled.

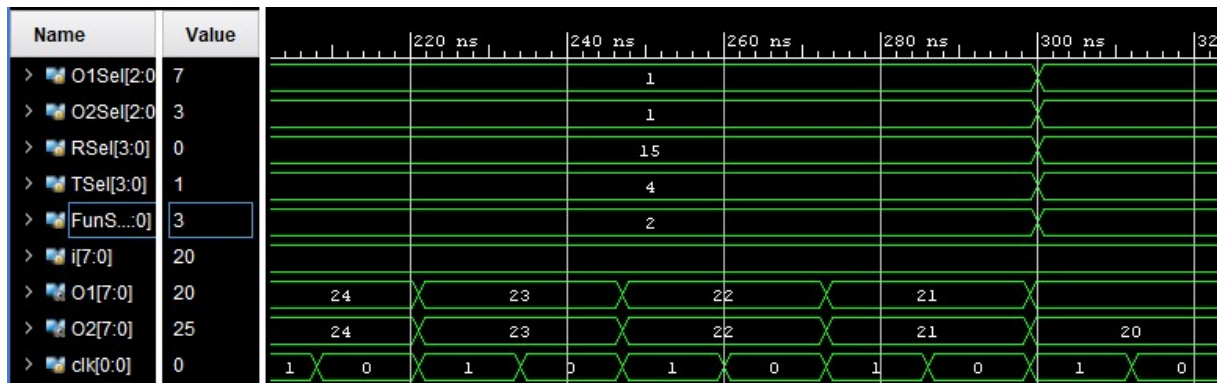


Figure 13: Decrement Test (part 2b)

Disabling every general purpose register and enabling only T4. Selecting R4 for O1 and T4 for O2 outputs. With these conditions, only O2 should change its value at first because it was disabled before decrement. After that clock signal, only O2 should increment.

 


Figure 14: Deactivate Register and Switch Output Test (part 2b)

Testing clearing while all registers are enabled.

 


Figure 15: Reset Test (part2b)

All conducted tests are as below.


 


Figure 16: Simulation Diagram As a Whole (part 2b)

 2.2.3 Part 2c

Adress register file (ARF) contains four 8-bit registers, and has a single 8-bit input, two 8-bit output ports, two 2-bit selectors for the outputs, 2-bit function select input and 4-bit register enable select input:



(a) ARF diagram

```

part2c.v
3  module ARF(
4      input          clk,
5      input[7:0]     i,
6      input[1:0]     out_b_sel,
7      input[1:0]     out_a_sel,
8      input[1:0]     funsel,
9      input[3:0]     r_sel,
10     output reg[7:0] out_a,
11     output reg[7:0] out_b
12 );
13

```

(b) Module definition in Verilog

Output selectors choose which register's data is shown on the corresponding port:

OutASel	OutA	OutBSel	OutB
00	AR	00	AR
01	SP	01	SP
10	PCPrev	10	PCPrev
11	PC	11	PC

Results of the address register file's simulation have a complex and not easy to follow waveform, since all of the registers cannot be viewed at the same time and are shown one by one, by altering the OutASel and OutBSel. For this reason, only the testbench output generated with *\$display* and *\$write* functions is provided. For proper formatting and code readability, testbench has tasks such as *displayHead* (prints table header containing port names), *showRegistersThroughA* and *showRegistersThroughB* (show the contents of all registers through port A and port B), *displayLine* and *showAll* (calls all task described at once). Also, tests with different parameters can be easily regenerated, because **Input** and **RSel** come as random values.

```
Testing adress register file (ARF)
```

```
Clear test
```

	Input	FunSel	RSel	AR	SP	PCPrev	PC
A:	xx	00	1111	00	00	00	00
B:	xx	00	0000	00	00	00	00

```
Load with random numbers test:
```

	Input	FunSel	RSel	AR	SP	PCPrev	PC
A:	21	01	1000	21	00	00	00
B:	21	01	0000	21	00	00	00

	Input	FunSel	RSel	AR	SP	PCPrev	PC
A:	db	01	0100	21	db	00	00
B:	db	01	0000	21	db	00	00

	Input	FunSel	RSel	AR	SP	PCPrev	PC
A:	3a	01	0010	21	db	3a	00
B:	3a	01	0000	21	db	3a	00

	Input	FunSel	RSel	AR	SP	PCPrev	PC
A:	0d	01	0001	21	db	3a	0d
B:	0d	01	0000	21	db	3a	0d

Figure 18: Clear and load test (part 2c)

Increment with random numbers test:							
	Input	FunSel	RSel	AR	SP	PCPrev	PC
A:	0d	11	1110	22	dc	3b	0d
A:	0d	11	0010	22	dc	3c	0d
A:	0d	11	1110	23	dd	3d	0d
A:	0d	11	0011	23	dd	3e	0e
A:	0d	11	0111	23	de	3f	0f
A:	0d	11	0100	23	df	3f	0f
A:	0d	11	1110	24	e0	40	0f
A:	0d	11	0000	24	e0	40	0f
A:	0d	11	1000	25	e0	40	0f
A:	0d	11	0110	25	e1	41	0f
A:	0d	11	1101	26	e2	41	10
A:	0d	11	1100	27	e3	41	10
A:	0d	11	0000	27	e3	41	10
A:	0d	11	1110	28	e4	42	10
A:	0d	11	0110	28	e5	43	10

Figure 19: Increment test (part 2c)

Decrement with random numbers test:							
	Input	FunSel	RSel	AR	SP	PCPrev	PC
B:	0d	10	1111	27	e4	42	0f
B:	0d	10	1000	26	e4	42	0f
B:	0d	10	1110	25	e3	41	0f
B:	0d	10	1001	24	e3	41	0e
B:	0d	10	0110	24	e2	40	0e
B:	0d	10	1010	23	e2	3f	0e
B:	0d	10	1000	22	e2	3f	0e
B:	0d	10	1101	21	e1	3f	0d
B:	0d	10	0001	21	e1	3f	0c
B:	0d	10	0011	21	e1	3e	0b
B:	0d	10	1011	20	e1	3d	0a
B:	0d	10	1000	1f	e1	3d	0a
B:	0d	10	0010	1f	e1	3c	0a
B:	0d	10	0010	1f	e1	3b	0a
B:	0d	10	1011	1e	e1	3a	09

Figure 20: Decrement test (part 2c)

2.3 Part 3

The Arithmetic Logic Unit (ALU) module has six ports. The table below introduces those ports.

Port Type	Port Name	Bit Width	Description
input	A	8	First operand of the ALU
input	B	8	Second operand of the ALU
input	FunSel	4	Function Selector
input	CLK	1	Clock input
output	OutALU	8	The resultant binary after an operation
output	ZCNO	4	Status flags of the ALU

Table 1: List of ports of the "alu" module

The module applies one of the sixteen operations defined according to selector input. The operations can be divided into three main sections. Arithmetic operations, logic operations, and shift operations.

1. Arithmetic Operations

Op Code	Function	Description
0100	A + B	Addition
0101	A - B	Subtraction
0110	Compare A, B	Return A if A > B, else 0

Table 2: List of arithmetic operations

 


Figure 21: Simulation of arithmetic operations

Note that carry bit is added in addition operation. This allows 16-bit addition applicable. A subtraction operation is used to compare integers, flags are set according to that operation.

2. Logic Operations

Op Code	Function	Description
0000	A	Return A
0001	B	Return B
0010	\overline{A}	Complement of A
0011	\overline{B}	Complement of B
0111	$A \cdot B$	Bitwise AND
1000	$A + B$	Bitwise OR
1001	$\overline{(A \cdot B)}$	Bitwise NAND
1010	$A \oplus B$	Bitwise XOR

Table 3: List of logic operations

 


Figure 22: Simulation of logic operations

3. Shift Operations

Op Code	Function	Description
1011	LSL A	Logical left shift of the bits of A
1100	LSR B	Logical right shift of the bits of A
1101	ASL A	Arithmetic left shift
1110	ASR A	Arithmetic right shift
1111	CSR A	Circular right shift

Table 4: List of shift operations

 


Figure 23: Simulation of shift operations

Note that the content of the carry bit will be visible in the output after a CSR operation.

- The difference between the response times of OutALU and ZCNO is due to the delay of the register module employed during the implementation of the flag register.

2.4 Part 4

This part is simply a gathered up version of previous parts we did. Inputs for this module are as follows:

Multiplexers: MuxASel, MuxBSel, MuxCSel are used as selectors for corresponding multiplexers.

MUXSelA	MUXOutA	MUXSelB	MUXOutB	MUXSelC	MUXOutC
00	OutALU	00	OutALU	0	RF_O1
01	Memory Output	01	Memory Output	1	ARF_OutA
10	IROut(7-0)	10	IROut(7-0)		
11	ARF OutA	11	ARF OutA		

Register File: RF_OutASel is for O1Sel, RF_OutBSel is for O2Sel, RF_FunSel is for FunSel, RF_TSel is for RSel and RF_RSel is for RSel.

Arithmetic Logic Unit: ALU_FunSel is for FunSel.

Address Register File: ARF_OutASel is for out_a_sel, ARF_OutBSel is for out_b_sel, ARF_FunSel is for funsel, ARF_RSel is for r_sel.


Instruction Register: IR_Funsel is for funsel, IR_Enable is for e, IR_LH is for l_h.

Memory: Mem_WR is for wr, Mem_CS is for cs.

Clock: Same clock signal is connected to every module.

The other wires inside the system are connected as in the project description.

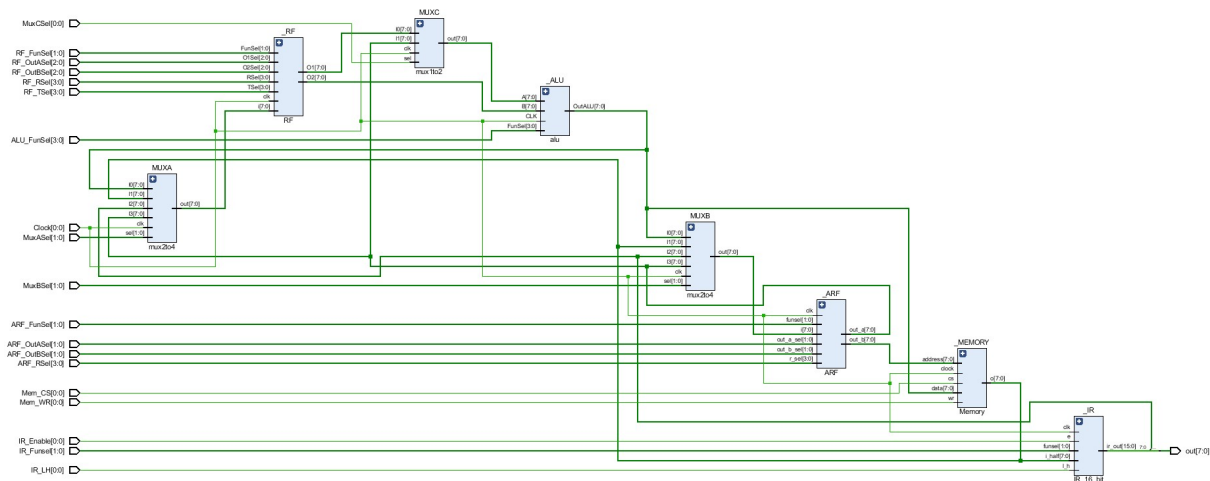The schematics of the implemented ALU system module is as below.



With the given simulation file and the testbench.mem file, inputs and corresponding outputs of our design are as follows.

Input Values:

Operation: 1

Register File: O1Sel: 4, O2Sel: 5, FunSel: 1, RSel: 12, TSel: 0

ALU FunSel: 3

Addres Register File: OutASel: 3, OutBSel: 3, FunSel: 3, Regsel: 15

Instruction Register: LH: 0, Enable: 0, FunSel: 0

Memory: WR: 0, CS: 1

MuxASel: 3, MuxBSel: 1, MuxCSel: 1

Output Values:

Register File: AOut: 0, BOut: 0

ALUOut: x, ALUOutFlag: 0, ALUOutFlags: Z:0, C:0, N:0, O:0,

Address Register File: AOut: 0, BOut (Address): 0

Memory Out: z

Instruction Register: IROut: 0

MuxAOut: 0, MuxBOut: z, MuxCOut: 0

Input Values:

Operation: 1

Register File: O1Sel: 4, O2Sel: 6, FunSel: 1, RSel: 10, TSel: 0

ALU FunSel: 12

Addres Register File: OutASel: 3, OutBSel: 3, FunSel: 3, Regsel: 15

Instruction Register: LH: 0, Enable: 0, FunSel: 0

Memory: WR: 0, CS: 1

MuxASel: 3, MuxBSel: 3, MuxCSel: 1

Output Values:

Register File: AOut: 1, BOut: 1

ALUOut: 255, ALUOutFlag: 2, ALUOutFlags: Z:0, C:0, N:1, O:0,

Address Register File: AOut: 1, BOut (Address): 1

Memory Out: z

Instruction Register: IROut: 0

MuxAOut: 1, MuxBOut: 1, MuxCOut: 1

3 tests completed.

3 Conclusion

In conclusion, this project has helped us gain a deeper understanding of basic computer and how it works. By designing each part as a module, we were able to reuse them in other parts, which made the project more efficient. Simulating each module for each combination of input allowed us to test the functionality of each part and ensure that they worked correctly. Overall, this project has been an excellent learning experience that has helped us develop our skills in basic computer organization and Verilog.