

ISTANBUL TECHNICAL UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT

BLG 222E
Computer Organization
Project Report

Project NO : 2
Due Date : 24.05.2023
GROUP NO : G37

GROUP MEMBERS:

150200075 : Matay AYDIN
150200096 : Mustafa KIRCI (Group Representative)
150200916 : Denis Iurie DAVIDOGLU

SPRING 2023

Contents

1	Introduction	1
2	Project	1
2.1	Design	1
2.2	Fetch Decode	1
2.3	Instructions	2
2.3.1	Sample Instruction	2
2.3.2	AND Instruction	3
2.3.3	OR Instruction	3
2.3.4	NOT Instruction	4
2.3.5	ADD Instruction	4
2.3.6	SUB Instruction	4
2.3.7	LSR Instruction	5
2.3.8	LSL Instruction	5
2.3.9	INC Instruction	5
2.3.10	DEC Instruction	6
2.3.11	BRA Instruction	6
2.3.12	BNE Instruction	7
2.3.13	MOV Instruction	7
2.3.14	LD Instruction	7
2.3.15	ST Instruction	8
2.3.16	PUL Instruction	8
2.3.17	PSH Instruction	9
3	Testing	9
4	Conclusion	18

1 Introduction

Computers can be different by their architecture, instruction sets, peripherals and performance. Although it seems like every architectures are doing the same thing, the way an operation executes could vary significantly under the hood. Some architectures could have limited number of instructions and others may have limited number of registers.

This project aims to implement a hardwired control unit and 16 instructions for CPU system using Verilog HDL. Control unit, as the name suggest, will modify control inputs of the ALU system according to the instructions it reads from the memory. The ALU system from project 1 will be used for arithmetic logic operations in this project.

2 Project

2.1 Design

CPU system is simply made out of 2 parts. Those are control unit and ALU system. Since ALU system implementation details are out of scope for this project, only control unit will be explained in detail.

Control unit is works in basically 2 parts. Those are fetch decode cycle and instruction cycle. Fetch and decode cycles have fixed number of clock cycles but number instruction cycles depend on the type of the instruction. Every cycle is explained in great detail below.

2.2 Fetch Decode

$T[0]: IR(0-7) \leftarrow M[PC]$

- Instruction register is enabled and its function is set to LOAD.
- Lower part(0-7) of the instruction register is selected.
- Memory is enabled and memory mode is set to read.
- Program counter is connected to memory address input.
- Only program counter and past program counter are enabled in address register file.
- Address register file function is set to INCREMENT.
- Every register in register file is disabled.
- Sequence counter function is set to INCREMENT.

T[1]: $IR(8-15) \leftarrow M[PC]$

- Instruction register is enabled and its function is set to LOAD.
- Upper part(8-15) of the instruction register is selected.
- Memory is enabled and memory mode is set to read.
- Program counter is connected to memory address input.
- Only program counter and past program counter are enabled in address register file.
- Address register file function is set to INCREMENT.
- Every register in register file is disabled.
- Sequence counter function is set to INCREMENT.

T[2]

- Memory is disabled
- Sequence counter function is set to INCREMENT.
- Every register in the CPU except sequence counter register is disabled.

2.3 Instructions

Every instruction is implemented into an if block and that if block will execute only if the corresponding decoded instruction op code is evaluated to 1. How every instruction gets executed is explained below.

2.3.1 Sample Instruction

To better illustrate the operation, the indices of x, y, and z are assigned to decoder signals, and the indices of a, b, and c are assigned to the register of the corresponding register file.

- $x, y, z \in [0, 3]; a = x, b = y, c = z$

$$T_3K_0S1_xS2_yD_z : (RF)R_c \leftarrow (RF)R_a \wedge (RF)R_b, SC \leftarrow 0$$

$$[(RF)FunSel = 01, MuxCSel = 1, O1 = (4 + x)_2, O2 = (4 + y)_2]$$

- $x, y \in [0, 3], z \in [4, 7]; a = x, b = y, c = z - 4$

$$T_3K_0S1_xS2_yD_z : (ARF)R_c \leftarrow (RF)R_a \wedge (RF)R_b, SC \leftarrow 0$$

$$[(ARF)FunSel = 01, MuxCSel = 1, O1 = (4 + x)_2, O2 = (4 + y)_2]$$

- $y \in [0, 3], x, z \in [4, 7]; a = x - 4, b = y, c = z - 4$

$$T_3K_0S1_xS2_yD_z : (ARF)R_c \leftarrow (ARF)R_a \wedge (RF)R_b, SC \leftarrow 0$$

$$[(ARF)FunSel = 01, MuxCSel = 0, OutA = (x)_2, O2 = (4 + y)_2]$$

- $y, z \in [0, 3], x \in [4, 7]; a = x - 4, b = y, c = z$

$$T_3K_0S1_xS2_yD_z : (RF)R_c \leftarrow (ARF)R_a \wedge (RF)R_b, SC \leftarrow 0$$

$$[(RF)FunSel = 01, MuxCSel = 0, OutA = (x)_2, O2 = (4 + y)_2]$$

Control signals that are common in all cases are listed below:

$$[(ALU)FunSel = 0111, MuxASel = 00, MuxBSel = 00, MemCS = 1, IR_E = 0]$$

2.3.2 AND Instruction

T[3] && K[0]: DSTREG \leftarrow SREG1 AND SREG2

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.
- Source register 1 and source register 2 are connected from corresponding module's output to ALU's input.
- ALU's function is set to AND.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.3 OR Instruction

T[3] && K[1]: DSTREG \leftarrow SREG1 OR SREG2

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.

- Source register 1 and source register 2 are connected from corresponding module's output to ALU's input.
- ALU's function is set to OR.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.4 NOT Instruction

T[3] && K[2]: DSTREG \leftarrow NOT SREG

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.
- Source register is connected from corresponding module's output to ALU's input.
- ALU's function is set to NOT.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.5 ADD Instruction

T[3] && K[3]: DSTREG \leftarrow SREG1 ADD SREG2

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.
- Source register 1 and source register 2 are connected from corresponding module's output to ALU's input.
- ALU's function is set to ADD.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.6 SUB Instruction

T[3] && K[4]: DSTREG \leftarrow SREG1 SUB SREG2

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.

- Source register 1 and source register 2 are connected from corresponding module's output to ALU's input.
- ALU's function is set to SUB.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.7 LSR Instruction

T[3] && K[5]: DSTREG \leftarrow LSR SREG

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.
- Source register is connected from corresponding module's output to ALU's input.
- ALU's function is set to LSR.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.8 LSL Instruction

T[3] && K[6]: DSTREG \leftarrow LSL SREG

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.
- Source register is connected from corresponding module's output to ALU's input.
- ALU's function is set to LSL.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.9 INC Instruction

T[3] && K[7]: DSTREG \leftarrow SREG

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.

- Source register is connected from corresponding module's output to ALU's input.
- ALU's function is set to A (NO_CHANGE).
- Memory is disabled and instruction register is disabled.

T[4] && K[7]: $\text{DSTREG} \leftarrow \text{DSTREG} + 1$

- Corresponding module of destination register's function is selected to INCREMENT.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.10 DEC Instruction

T[3] && K[8]: $\text{DSTREG} \leftarrow \text{SREG}$

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.
- Source register is connected from corresponding module's output to ALU's input.
- ALU's function is set to A (NO_CHANGE).
- Memory is disabled and instruction register is disabled.

T[4] && K[8]: $\text{DSTREG} \leftarrow \text{DSTREG} - 1$

- Corresponding module of destination register's function is selected to DECREMENT.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.11 BRA Instruction

T[3] && K[9]: $\text{PC} \leftarrow \text{VALUE}$

- Register file registers are disabled.
- Address register file input is connected to input register output (value).
- PC register is enabled in Address register file.
- Address register file function is set to LOAD.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.12 BNE Instruction

T[3] && K[10]: IF Z == 0: PC \leftarrow VALUE

- Register file registers are disabled.
- Address register file input is connected to input register output (value).
- PC register is enabled in Address register file.
- Address register file function is set to LOAD.
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

T[3] && K[10]: IF Z == 1: PC \leftarrow VALUE

- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.13 MOV Instruction

T[3] && K[11]: DSTREG \leftarrow SREG

- MUXA and MUXB are set to select output of ALU.
- Destination registers are enabled and their corresponding module's function is set to LOAD.
- Source register is connected from corresponding module's output to ALU's input.
- ALU's function is set to A or B depending on the source register (NO_CHANGE).
- Memory is disabled, sequence counter is cleared and instruction register is disabled.

2.3.14 LD Instruction

T[3] && K[12]: Rx \leftarrow VALUE

- Corresponding Rx in register file is enabled.
- Register file function is set to LOAD.
- If I is 0 (immediate address):

Register file input is connected to instruction register's output.

- If I is 1 (direct address):

Register file input is connected to the memory output.

Memory address input is connected to address register in address register file.

Memory is enabled and memory mode is set to READ.

- Every register in address register file is disabled.
- Sequence counter is cleared and instruction register is disabled.

2.3.15 ST Instruction

T[3] && K[13]: $\text{VALUE} \leftarrow \text{Rx}$

- Memory is enabled and memory mode is set to WRITE.
- Memory address input is connected to address register in address register file.
- Memory input is connected to ALU's output.
- ALU's B input is connected to Rx.
- ALU's function is set to B (NO_CHANGE).
- Every register in address register file is disabled.
- Sequence counter is cleared and instruction register is disabled.

2.3.16 PUL Instruction

T[3] && K[14]: $\text{SP} \leftarrow \text{SP} + 1, \text{Rx} \leftarrow \text{M}[\text{SP}]$

- Register file input is connected to memory output.
- Only Rx is enabled in register file.
- Register file function is set to LOAD.
- Memory address input is connected to address register in address register file.
- Memory is enabled and memory mode is set to READ.
- Stack pointer in address register file is enabled.
- Address register file function is set to INCREMENT.
- Sequence counter is cleared and instruction register is disabled.

2.3.17 PSH Instruction

T[3] && K[15]: $SP \leftarrow SP - 1$

- Memory mode is set to read.
- Only stack pointer in the address register file is enabled.
- Address register file function is set to DECREMENT.
- Instruction register is disabled.

T[4] && K[15]: $M[SP] \leftarrow Rx$

- Memory is enabled and memory mode is set to WRITE.
- Memory address input is connected to stack pointer register.
- Every register in address file register is disabled.
- ALU's input is connected to Rx in the register file.
- ALU's function is set to Rx (B, NO_CHANGE) and connected to memory input.
- Sequence counter is cleared and instruction register is disabled.

3 Testing

Trying instructions on their own is not enough to ensure the overall proper function of our computer with more complex programs. Therefore, we developed an assembler in C programming language, which parses an assembly program, finds labels, calculates the correct positions in memory, translates all symbols to machine code and outputs binary and hexadecimal **.mem** files. Our assembler ignores all vertical and horizontal white-space, as well as the comments inserted by the **#** symbol. It can also recognize some errors in the assembly code and print error messages. It has two pseudo-instructions, **ORG** and **END**, and an extra instruction **HLT**, which was implemented in the Verilog design as well. **ORG** takes a hexadecimal value as a parameter, which represents the address location of the next instruction. Therefore, it is easy for a programmer to describe the contents of different parts of memory. **END** is optional, and it tells the assembler to stop at that line and to not process anything after it. Finally, the extra **HLT** instruction is important because it makes the machine stop execution and allow inspecting the results. In memory, it has hexadecimal value of 0xFFFF, and this value is checked by the control unit after the fetch and decode cycle. If the halt instruction is detected, then

`$writememh` and `$finish` is called in Verilog.

```
C assembler.c x
assembler > C assembler.c > [O] OpcodeTable
368 //printf("%s\n", hex_buffer);
369 fprintf(memory_file, "%c%c\n%c%c\n", hex_buffer[2], hex_buffer[3], hex_buffer[0], hex_buffer[1]);
370 for (int j = 8; j < 16; j++)
371     fprintf(bin_memory_file, "%d", BIN_RAM[i][j]);
372 fprintf(bin_memory_file, "\n");
373 for (int j = 0; j < 8; j++)
374     fprintf(bin_memory_file, "%d", BIN_RAM[i][j]);
375 fprintf(bin_memory_file, "\n");
376 }
377
378 fclose(assembly_file);
379 fclose(memory_file);
380 fclose(bin_memory_file);
381
382 printf("RAM.mem and BIN_RAM.mem were created.\n");
383 if (!has_hlt)
384     printf("Warning, the program does not have a HLT instruction\n");
385 return 0;
386 }
```


Last lines of our assembler program

The simple loop example given in the assignment was slightly modified and automatically assembled. Modifications include adding previously mentioned custom instructions, removing address mode specifiers for all instructions except LD (because it is the only one which does offer to choose the addressing mode), as well as assigning locations between 0xB0 and 0xBA with some data.


```

1      BRA 0x28    # This instruction is written to the memory address 0x00,
2                  # The first instruction must be written to the address 0x28
3
4      ORG 0x28
5      LD R1 IM 0x0A # This first instruction is written to the address 0x28,
6                  # R1 is used for iteration number
7      LD R2 IM 0x00 # R2 is used to store total
8      LD R3 IM 0xB0
9      MOV AR R3    # AR is used to track data address: starts from 0xB0
10 LABEL: LD R3 D    # R3    M[AR] (AR = 0xB0 to 0xBA)
11      ADD R2 R2 R3 # R2    R2 + R3 (Total = Total + M[AR])
12      INC AR AR    # AR    AR + 1 (Next Data)
13      DEC R1 R1    # R1    R1    1 (Decrement Iteration Counter)
14      BNE LABEL # Go back to LABEL if Z=0 (Iteration Counter > 0)
15      INC AR AR    # AR    AR + 1 (Total will be written to 0xBB)
16      ST R2        # M[AR]    R2 (Store Total at 0xBB)
17      HLT
18
19      ORG 0xB0 # place some values at 0xB0
20      0x01
21      0x02
22      0x03
23      0x04
24      0x05
25      END

```

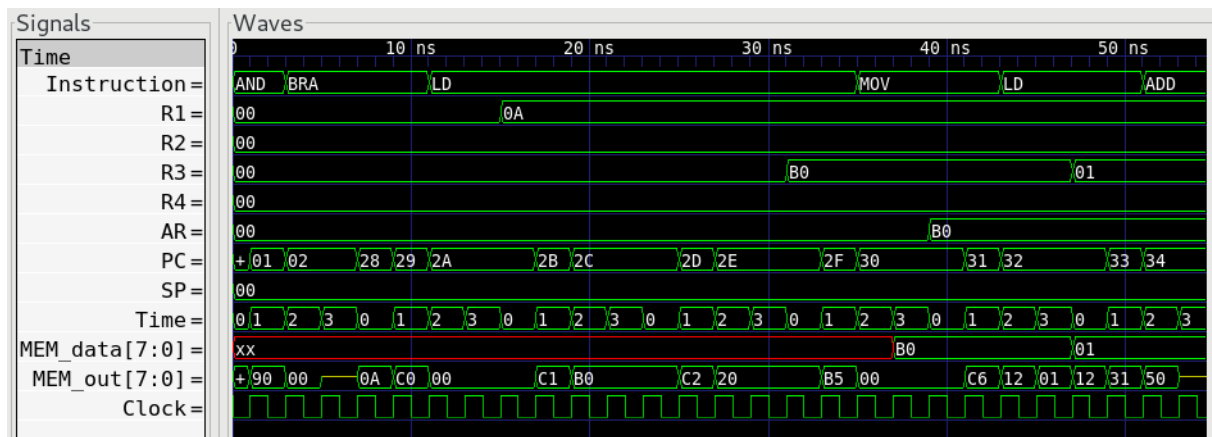

(a) Beginning of execution

 

(b) End of execution

```

--- RAM.mem      2023-05-23
+++ RAM OUT.mem  2023-05-23
@@ -197,7 +197,7 @@
05
00
00
-00
+0f
00
00
00

```

(c) Differences in memory

Loop example program's results

After the execution, our computer writes 0x0F to the memory, which is indeed the sum of values between the addresses 0xB0 and 0xBA.

As an example from our part, we present a solution to a LeetCode easy question in our computer's assembly language:

```

1 # https://leetcode.com/problems/search-insert-position/
2 # Given a sorted array of distinct integers and a target value,
3 # return the index if the target is found. If not, return the
4 # index where it would be if it were inserted in order.
5
6 ORG 0x0
7 # initialize the stack
8 LD R1 IM 0xFF
9 MOV SP R1
10 # load the target to R1
11 LD R1 IM TARGET
12 MOV AR R1
13 LD R1 D
14 # load the array pointer to AR
15 LD R2 IM ARRAY
16 MOV AR R2
17
18 LOOP_1:   BRA IS_SMALLER
19 RETURN:   PUL R3 # take the result of the function
20           LD R4 IM 0x01 # check if true
21           SUB R2 R3 R4
22           BNE CONTINUE_3
23           BRA EXIT
24 CONTINUE_3: INC AR AR
25             INC AR AR
26             # check if the end of array is reached
27             LD R3 D
28             MOV R3 R3
29             BNE LOOP_1
30             BRA EXIT
31
32 # R1 - Target, R2 - Value-to-Compare, R3 - Limit, R4 - Guessing Pointer
33 IS_SMALLER: MOV R4 R1      # set the guessing pointer as the target initially
34 LOOP_2:     LD R2 D         # R2 stores the value currently pointed
35             SUB R3 R2 R4
36             BNE CONTINUE_1
37             BRA RETURN_TRUE # if guessing pointer reaches the value-to-compare

```

```

38                                     # before overflow, the result is true
39 CONTINUE_1: LD R3 IM 0xFF # store limit
40             SUB R2 R3 R4
41             BNE CONTINUE_2
42             BRA RETURN_FALSE # if guessing pointer reaches the limit without
43                                     # finding the value-to-compare, the result is false
44 CONTINUE_2: INC R4 R4
45             BRA LOOP_2
46 RETURN_FALSE: LD R3 IM 0x00
47               PSH R3 # push false
48               BRA RETURN
49 RETURN_TRUE:  LD R3 IM 0x01
50               PSH R3 # push true
51               BRA RETURN
52
53             # save result
54 EXIT: LD R1 IM ARRAY
55       SUB R1 AR R1
56       LSR R1 R1
57       INC R1 R1
58       LD R2 IM RESULT
59       MOV AR R2
60       ST R1
61       # clear stack
62       LD R1 IM 0x00
63       PSH R1
64       PUL R1
65       HLT
66
67       ORG 0xD0
68 TARGET: 0x99
69 ARRAY: 0x13
70        0x15
71        0x3A
72        0x51
73        0x58
74        0x9E
75        0xA5
76 RESULT: 0x00
77       END

```


To find a specific element in an array, one must be able to compare the values. However, in our instruction set we have just one conditional branch, the BNE instruction, which branches if the ALU output is not zero. The program would have been much shorter if we made use of hardware optimization. Instead, we wrote a subroutine called IS_SMALLER, which compares the registers R1 and R2, and pushes either true or false to the stack. Later in the main loop, the returned value is pulled and decisions are made. The main loop continues to search for a suitable position in array, and when it finds, the program jumps to the EXIT routine. There, some operations are performed before the output can be stored. The value returned by the program is the index where the target was found or can be inserted, with one as the first index of the array. The program functions correctly as it can be seen from the figures below:

The screenshot shows an IDE with two panels. The left panel displays the assembly code for `search_insert_position.asm`. The right panel shows the terminal output of running the program.

Assembly Code (Left Panel):

```

67      ORG 0xD0
68  TARGET: 0x00
69  ARRAY: 0x13
70      0x15
71      0x3A
72      0x51
73      0x58
74      0x9E
75      0xA5
76  RESULT: 0x00
77      END

```

Terminal Output (Right Panel):

```

dawidogg@debian11: ~/Documents/storageD/ITU/4thseme
dawidogg@debian11:~/Documents/storageD/ITU/4thseme
jects/Project1$ ./run search_insert_position.asm
VCD info: dumpfile dump.vcd opened for output.
control_unit.v:166: $finish called at 1511000 (1ps)
--- RAM.mem      2023-05-24 02:43:03.048344596 +0300
+++ RAM_OUT.mem  2023-05-24 02:43:03.276347026 +0300
@@ -237,7 +237,7 @@
a5
00
// 0x000000e0
-00
+01
00
00
00

```

Test with input 0x00. Since it is the smallest, it should be inserted to the first position.

Line	Code	Output
67	ORG 0xD0	
68	TARGET: 0x13	
69	ARRAY: 0x13	
70	0x15	
71	0x3A	
72	0x51	
73	0x58	
74	0x9E	
75	0xA5	
76	RESULT: 0x00	
77	END	

```

dawidogg@debian11: ~/Documents/storageD/ITU/4thseme
dawidogg@debian11:~/Documents/storageD/ITU/4thseme
jects/Project1$ ./run search_insert_position.asm
VCD info: dumpfile dump.vcd opened for output.
control_unit.v:166: $finish called at 257000 (1ps)
--- RAM.mem      2023-05-24 02:44:08.141036679 +0300
+++ RAM_OUT.mem  2023-05-24 02:44:08.281038165 +0300
@@ -237,7 +237,7 @@
a5
00
// 0x000000e0
-00
+01
00
00
00

```

Test with input 0x13. Here we found the target, and the result is its position, one.

Line	Code	Output
67	ORG 0xD0	
68	TARGET: 0x14	
69	ARRAY: 0x13	
70	0x15	
71	0x3A	
72	0x51	
73	0x58	
74	0x9E	
75	0xA5	
76	RESULT: 0x00	
77	END	

```

dawidogg@debian11: ~/Documents/storageD/ITU/4thseme
dawidogg@debian11:~/Documents/storageD/ITU/4thseme
jects/Project1$ ./run search_insert_position.asm
VCD info: dumpfile dump.vcd opened for output.
control_unit.v:166: $finish called at 16007000 (1ps
--- RAM.mem      2023-05-24 02:44:40.357377975 +0300
+++ RAM_OUT.mem  2023-05-24 02:44:41.285387794 +0300
@@ -237,7 +237,7 @@
a5
00
// 0x000000e0
-00
+02
00
00
00

```

Test with input 0x14. Target is placed between 0x13 and 0x15, and gets the second position.

Line	Code
67	ORG 0xD0
68	TARGET: 0x53
69	ARRAY: 0x13
70	0x15
71	0x3A
72	0x51
73	0x58
74	0x9E
75	0xA5
76	RESULT: 0x00
77	END

```

dawidogg@debian11: ~/Documents/storageD/ITU/4thseme
dawidogg@debian11:~/Documents/storageD/ITU/4thseme
jects/Project1$ ./run search_insert_position.asm
VCD info: dumpfile dump.vcd opened for output.
control_unit.v:166: $finish called at 46691000 (1ps)
--- RAM.mem      2023-05-24 02:45:16.909764296 +0300
+++ RAM_OUT.mem  2023-05-24 02:45:19.405790641 +0300
@@ -237,7 +237,7 @@
a5
00
// 0x000000e0
-00
+05
00
00
00

```

Test with input 0x53. Output is the 5th position.


Line	Code
67	ORG 0xD0
68	TARGET: 0xFF
69	ARRAY: 0x13
70	0x15
71	0x3A
72	0x51
73	0x58
74	0x9E
75	0xA5
76	RESULT: 0x00
77	END

```

dawidogg@debian11: ~/Documents/storageD/ITU/4thseme
dawidogg@debian11:~/Documents/storageD/ITU/4thseme
jects/Project1$ ./run search_insert_position.asm
VCD info: dumpfile dump.vcd opened for output.
control_unit.v:166: $finish called at 1369000 (1ps)
--- RAM.mem      2023-05-24 02:46:39.234631148 +0300
+++ RAM_OUT.mem  2023-05-24 02:46:39.442633334 +0300
@@ -237,7 +237,7 @@
a5
00
// 0x000000e0
-00
+08
00
00
00

```

 Test with input 0xFF. It is the biggest value, so it is placed to the end of array, at the 8th position.



Waveform at the moment when the output is stored.

4 Conclusion

In conclusion, this project helped us gain a deeper understanding of basic computer and how it works. By designing our own control unit, we were able to implement our instructions. To test our implementations, we created machine codes for input and evaluated the results of each instruction. Overall, this project has been an excellent learning experience that has helped us develop our skills in basic computer organization and Verilog.